

# Array Multiplier

- Author: Will Shang, Tyler Huynh
- Description: 4x4 Array Multiplier that multiplies two four-bit numbers
- Language: Verilog

## How it works

This project uses a 4x4 Array Multiplier to multiply two four-bit numbers together, using a series of full adders to result in an 8 bit product (figure 1). The multiplier works by systematically multiplying each bit of the first number with each bit of the second number. These partial products are then combined using a series of full adders to form the final result.

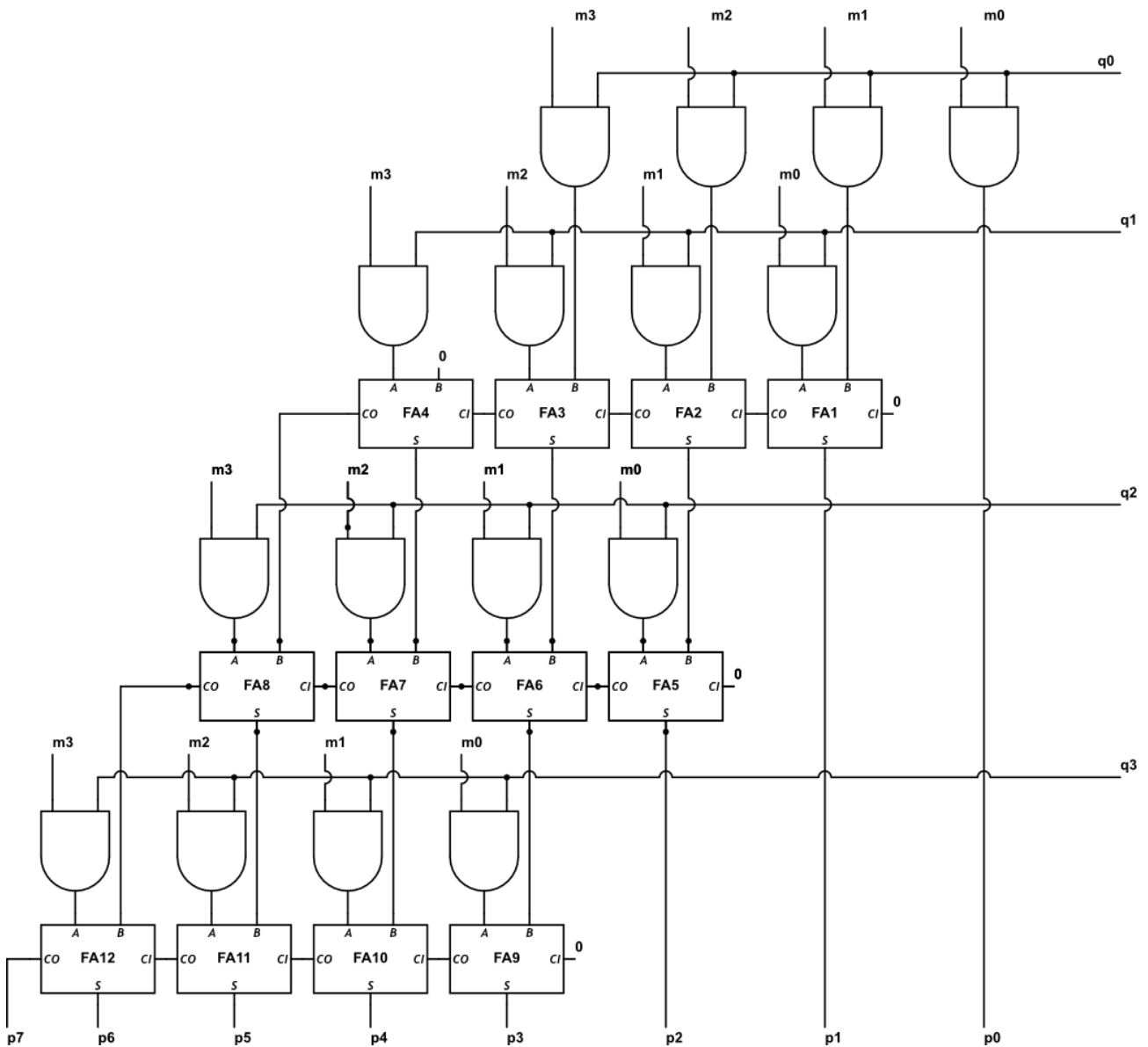


Figure 1: 4x4 Array Multiplier

## How to test

Input two 4-bit binary numbers and manually verify the output. For example: 1st num: 1001 2nd num: 1011 Output: 1100011 (binary), or 0x63 (hexadecimal) The format of the output can be adjusted in test.py, but the value they represent should be accurate to the product of the two 4-bit binary numbers.

## Pinout

| # | Input | Output | Bidirectional |
|---|-------|--------|---------------|
| 0 | m[0]  | p[0]   |               |
| 1 | m[1]  | p[1]   |               |
| 2 | m[2]  | p[2]   |               |
| 3 | m[3]  | p[3]   |               |
| 4 | q[0]  | p[4]   |               |
| 5 | q[1]  | p[5]   |               |
| 6 | q[2]  | p[6]   |               |
| 7 | q[3]  | p[7]   |               |